

Roll No.

[illegible]

Odd Semester Examination-2016

**B.Tech. (Semester-III)** EC FCS

# DIGITAL ELECTRONICS AND DESIGN ASPECTS

**[Time : 3 Hours]**

**[Maximum Marks :100]**

**Note :** Attempt all questions.

1. Attempt **any four** parts of the following : [5x4 = 20]
- (a) Determine the base 'b' in each of the following cases:
- (i)  $(361)_{10} = (551)_b$
- (ii)  $(859)_{10} = (5B7)_b$
- (b) Define Hamming code of error detection. Obtain 7-bit Hamming code for the message signal 1101 by using even parity.
- (c) Using K-Map simplify the following expression:
- $f(A, B, C, D) = \sum_m (0, 1, 3, 7, 9, 11, 12)$

TEC-302/820

(1)

[P.T.O.]

(d) Explain Even and Odd parity methods for the detection of 1-bit binary error.

(e) Convert the following numbers to the base as indicated:

(i)  $(101101)_2 = (?)_{10}$

(ii)  $(56)_{10} = (?)_8$

(iii)  $(A46)_{16} = (?)_2$

52 (f) Convert the following expressions to the canonical form:

(i)  $F = AB' + A'C + A$

(ii)  $F = (A + B)(B' + C)$

2. Attempt any four parts of the following : [5×4=20]

(a) Design a 32:1 Mux by using 8:1 Mux and 4:1 Mux.

(b) Implement the following function by using 8:1 Mux

$$f(A, B, C, D) = \sum_m (0, 1, 2, 4, 7, 11, 12, 13, 15)$$

(c) Explain the working of 3:8 Decoder.

(d) What are the differences between normal encoder and priority encoder? Design a 4-input priority encoder.

(e) Design a 4-input combinational circuit that converts binary code to gray code.

(f) What are the drawbacks of a full adder? Explain how a parallel adder removes the drawback of a full adder?



Attempt **any two** parts of the following : [10×2=20]

(a) (i) What is Race-Around condition? Explain the master-slave flip-flop.

(ii) Analyze the circuit shown in fig. 1 to produce Boolean algebraic expression for the circuit outputs.

13

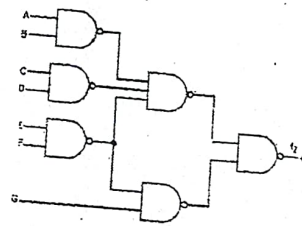


Fig. 1

(b) Explain the basic working of JK Flip-Flop. Design D Flip-Flop using JK Flip-Flop.

(c) Differentiate synchronous and asynchronous sequential circuit. Design a synchronous counter

TEC-302/820

(3)

[P.T.O.]

161