

**BASIC ELECTRICAL ENGINEERING**

**2<sup>nd</sup> Exam/ECE/ECE-II/ETV/COMP/IT/CSc/EEE/0064/May'18**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Do as directed.**

**10x1.5=15**

- Unit of resistance is \_\_\_\_\_.
- Define ohms law.
- In domestic installation all the electrical appliances are connected in \_\_\_\_\_
- Constant voltage source has \_\_\_\_\_ internal impedance as compared to external load impedance.
- Unit of magnetic flux density is \_\_\_\_\_
- The specific gravity of fully charged cell is \_\_\_\_\_
- Draw sinusoidal AC waveform w.r.t. angle.
- At resonance in series RLC circuit,  $X_L =$  \_\_\_\_\_
- The formula for calculating the capacitive reactance  $X_c =$  \_\_\_\_\_
- Fuel used in thermal power plant is \_\_\_\_\_

**SECTION-B**

**Q2. Attempt any six questions.**

**6x5=30**

- Define Resistance. On which factor resistance depends discuss.
- Resistance of 2ohm, 3ohm and 6ohm are connected in parallel and the combination is connected in series with a resistance of 1 ohm across a battery with an E.M.F. of 44V. find
  - Potential difference across 1ohm resistance.
  - Potential difference across parallel circuit.
  - Current in each resistor.
- Discuss comparison between magnetic and electric circuit.
- Write a short note on
  - Cycle
  - Time period
  - Frequency
  - Amplitude
  - Phase
- Discuss resistance inductance and capacitance in series
- What do you mean by Q factor of a parallel circuit? What is its importance?
- Discuss nuclear power station with neat diagram
- Discuss Kirchhoff's voltage law.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- State and explain the venin's theorem.
- Explain the construction and working of Lead acid battery.
- Explain the steam power plant with neat diagram
- Explain the generation of alternating voltage with diagram and discuss e.m.f. equation.